


Computer Organization

Assembling the Computer

Computer Implementation

- The HACK computer consists of 3 major components
 - ROM
 - CPU
 - RAM
- We can quite easily implement this using our previous chapters and a few provided chips

Computer Implementation – cont.

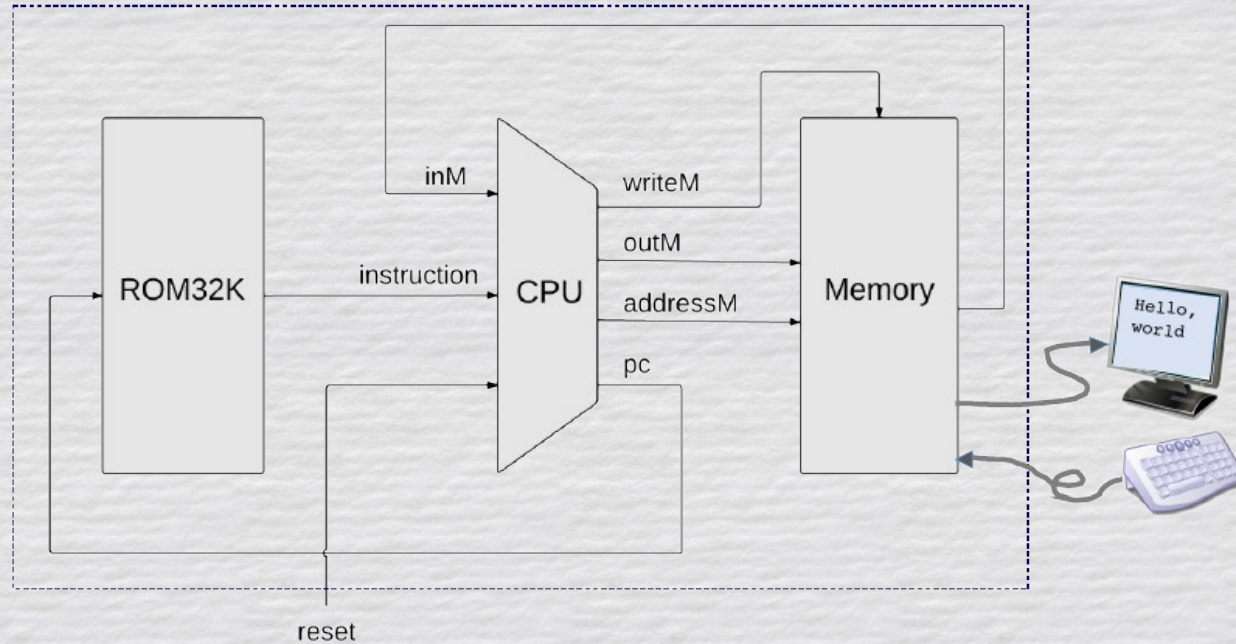


```
17 CHIP Computer {
18
19     IN reset;
20
21     PARTS:
22     ROM32K(address=pc,out=instruction);
23
24     CPU(instruction=instruction,reset=reset,
25         inM=inM,outM=outM,writeM=writeM,
26         addressM=addressM,pc=pc);
27
28     Memory(in=outM,load=writeM,address=addressM,
29         out=inM);
30 }
```

CPU

- The CPU is by far the most difficult component to implement
- It primarily consists of the ALU, A/D/PC Registers, and several basic gates for the logic reasons
- The best method to implement the chip is to break it down in several steps

Computer Implementation – cont.

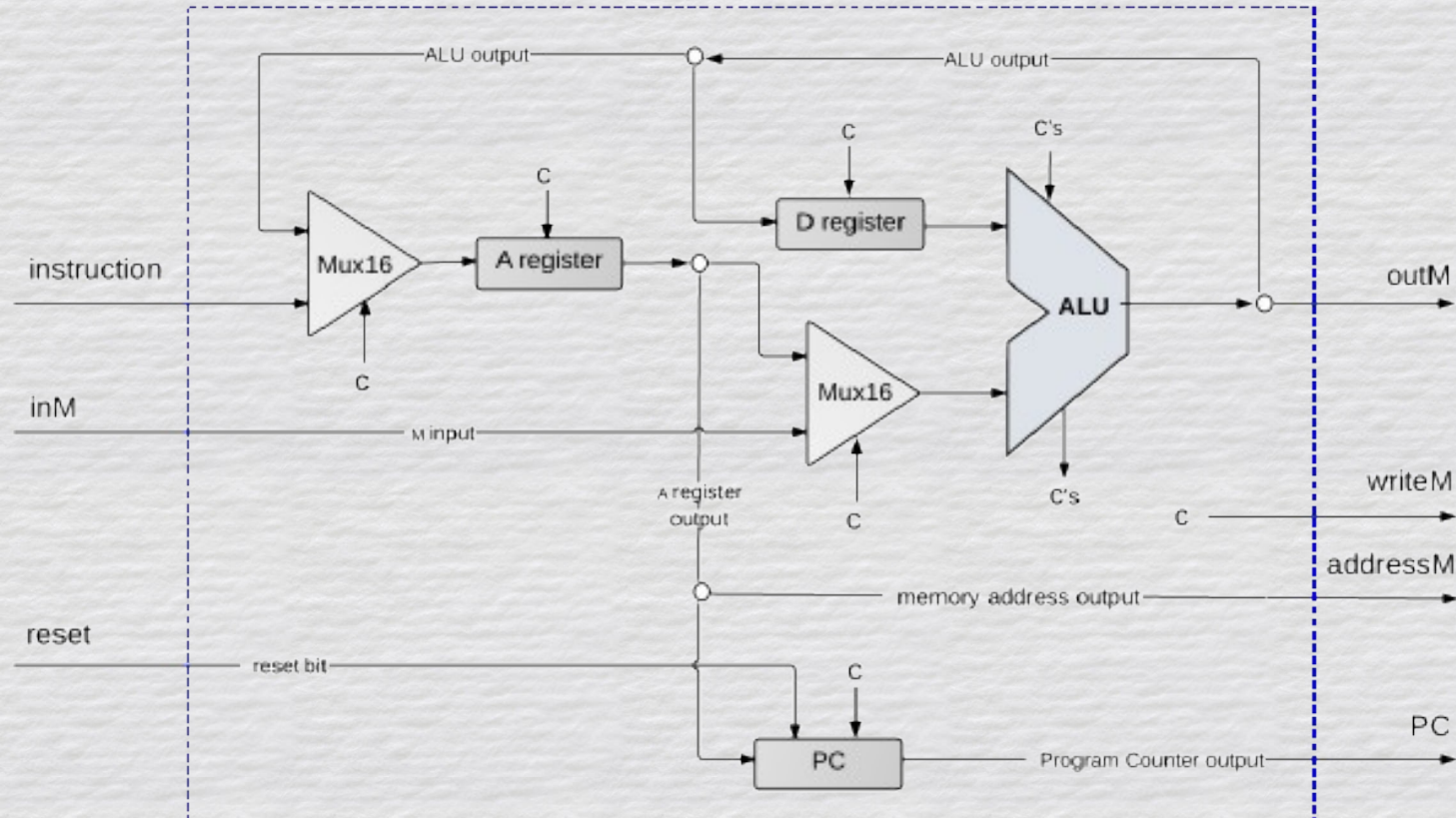

Instruction Bits

- Before we can begin implementing the CPU, we need to take a look at our main input: **The Instruction**
- The Instruction is a 16-bit input that is either an A or a C instruction
- We can use the previous chapter to understand how these instructions are setup


Instruction Bits – cont.

```
42      /*
43      instruction bits:
44          instruction[15] == Op-code bit (determines A or C instruction)
45          instruction[14] == Unused bit during C instructions
46          instruction[13] == Unused bit during C instructions
47          instruction[12] == A bit (determines if M register is used during ALU operation)
48          instruction[11] == ALU zx bit (c1 bit)
49          instruction[10] == ALU nx bit (c2 bit)
50          instruction[9] == ALU zy bit (c3 bit)
51          instruction[8] == ALU ny bit (c4 bit)
52          instruction[7] == ALU f bit (c5 bit)
53          instruction[6] == ALU no bit (c6 bit)
54          instruction[5] == A register bit (d1 bit)
55          instruction[4] == D register bit (d2 bit)
56          instruction[3] == M register bit (d3 bit)
57          instruction[2] == LT bit (j1 bit)
58          instruction[1] == EQ bit (j2 bit)
59          instruction[0] == GT bit (j3 bit)
60      */
```

Implementing the CPU

- Now that we have looked at the overview and the instruction bits, we can begin implementing the various components
 - A-Register
 - D-Register
 - M-Register
 - ALU
 - Jump bits
 - PC Register


A-Register

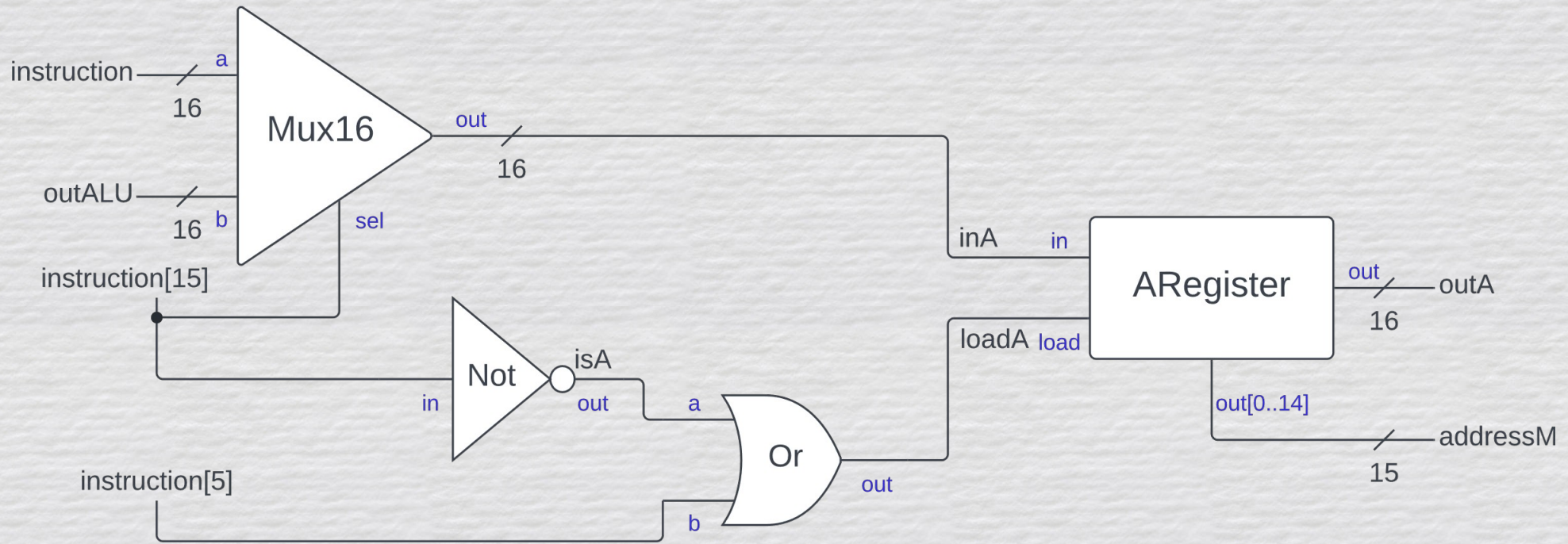

A-Register – Code

```
62 //=====
63 // A-Register
64 /*
65 |   Use the Op-Code to choose between a constant (A-Instruction)
66 |   and the ALU's output (C-Instruction) for the input to the
67 |   A-Register
68 */
69 Mux16(a=, b=, sel=, out=);
70
71 // Not the Op-Code to determine if an A-Instruction is being processed
72 Not(in=, out=);
73
74 /*
75 |   When !instruction[15] == 1, it is @value which means A should load a value
76 |   When instruction[5] == 1, it is A=outALU which means A should load a value
77 */
78 Or(a=, b=, out=);
79
80 /*
81 |   Loads a new input to the A-Register if above code dictates it to
82 |   Outputs both to A-Register and sets the memory address
83 */
84 ARegister(in=, load=, out=, out[0..14]=);
```


D-Register

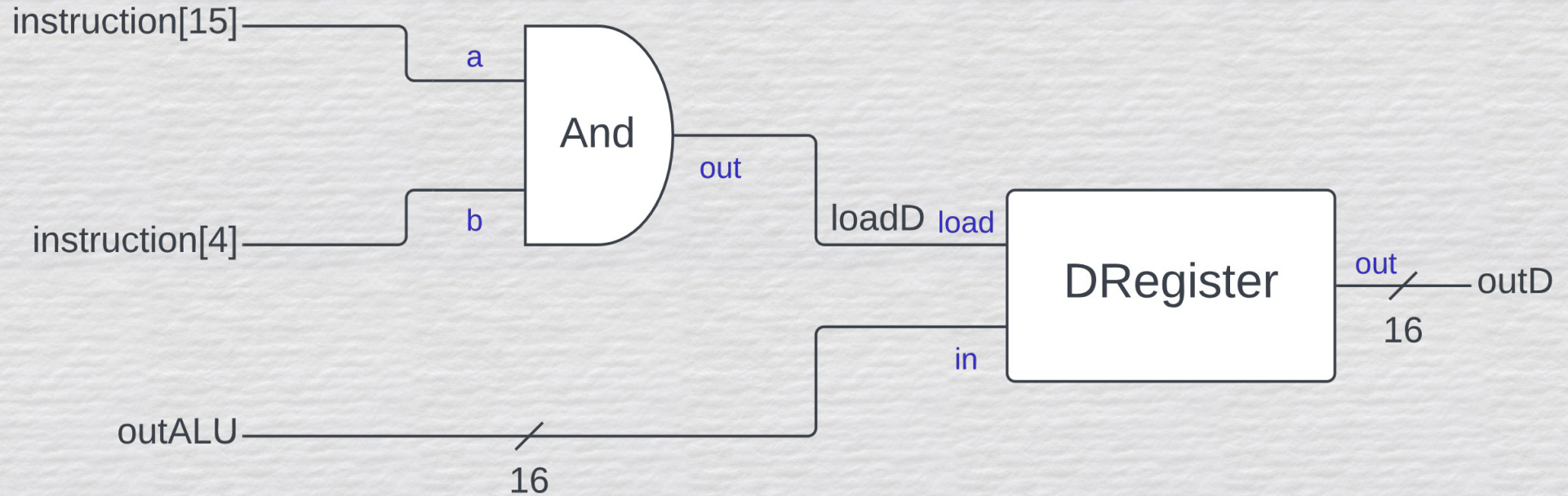

D-Register – Code

```
85 //=====
86 // D-Register
87 // When instruction[4] == 1, it is D=outALU which means D should load a value
88 And(a=, b=, out=);
89
90 /*
91 |   Loads a new input to the D-Register if above code dictates it to
92 |   Set the ALU x-input to D
93 */
94 DRegister(in=, load=, out=);
```


M-Register

 

M-Register – Code

```
96 //=====
97 // M-Register
98 // When instruction[3] == 1, it is M=outALU which means M should load a value
99 And(a=, b=, out=);
```


ALU

 




ALU – Code

```
101 //=====
102 // ALU
103 // Set the ALU y-input to either A or M (RAM[A])
104 Mux16(a=, b=, sel=, out=);
105
106 // Set the ALU appropriately
107 ALU(x=, y=, // Set the ALU inputs
108     zx=, nx=, // Set the X Pins
109     zy=, ny=, // Set the Y Pins
110     f=, no=, // Set the Function Pins
111     out=, out=, // Set the ALU Outputs
112     zr=, ng=); // Set the Output Flags
```


Jump – Pt. 1

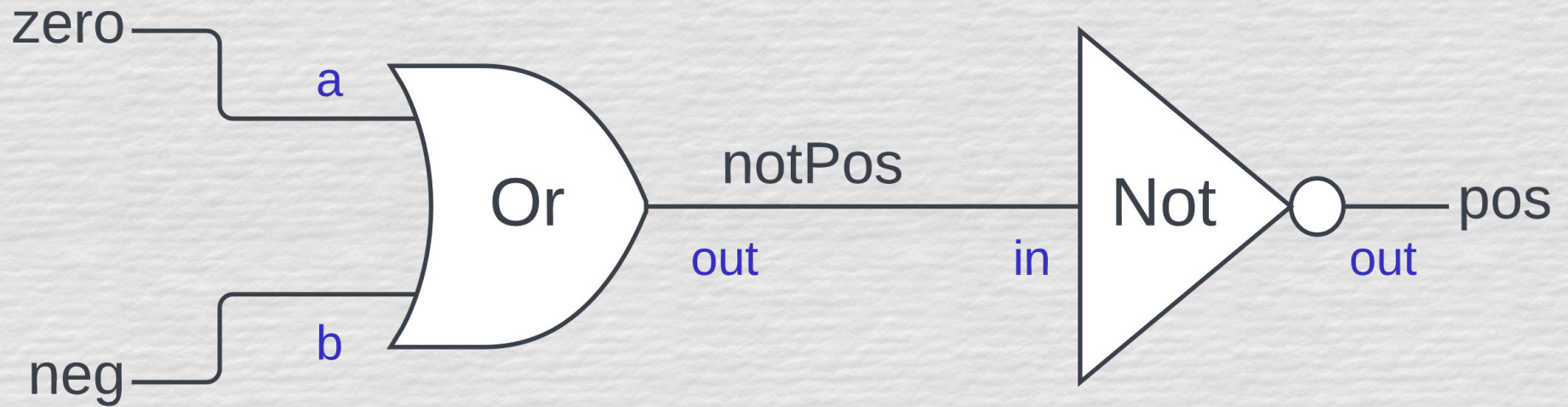

Jump – Pt. 2

   


Jump – Pt. 3

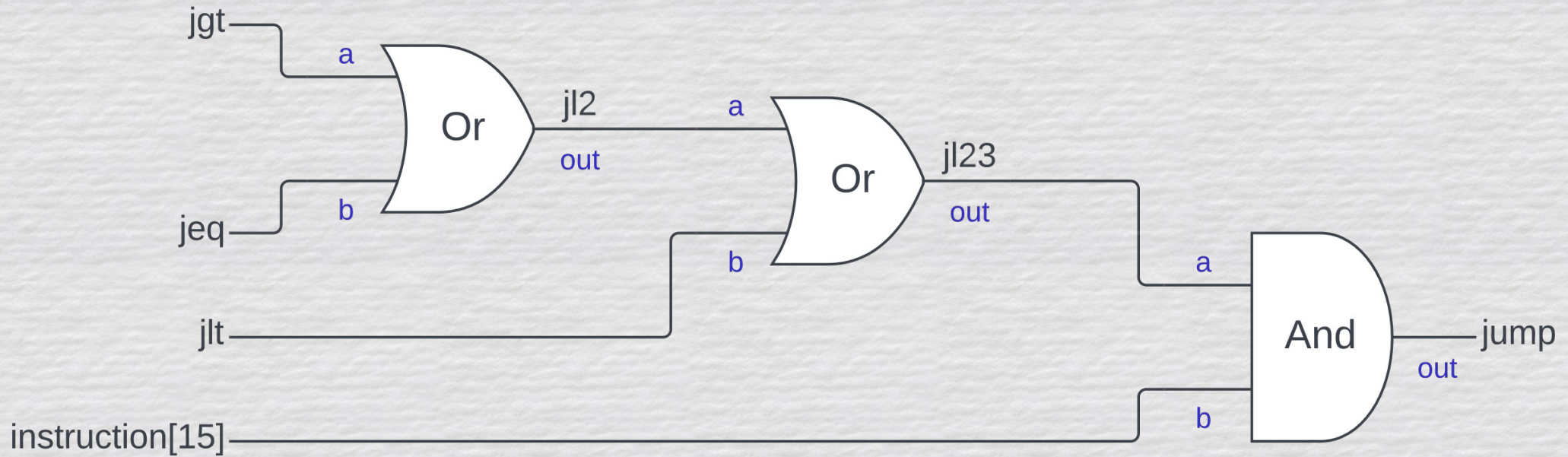

Jump – Code

```
114 //=====
115 // Jump
116 // zero | neg ALU flags to determine if neither is true
117 Or(a=, b=, out=);
118 // Negate the result to determine if positive is true
119 Not(in=, out=);
120
121 And(a=, b=, out=); // outALU > 0
122 And(a=, b=, out=); // outALU == 0
123 And(a=, b=, out=); // outALU < 0
124
125 // Combine the first 2 jump bits
126 Or(a=, b=, out=);
127 // Combine the prior jump bits and 3rd jump bit
128 Or(a=, b=, out=);
129
130 // When j123 == 1, the jump condition is met
131 And(a=, b=, out=);
```

PC Register

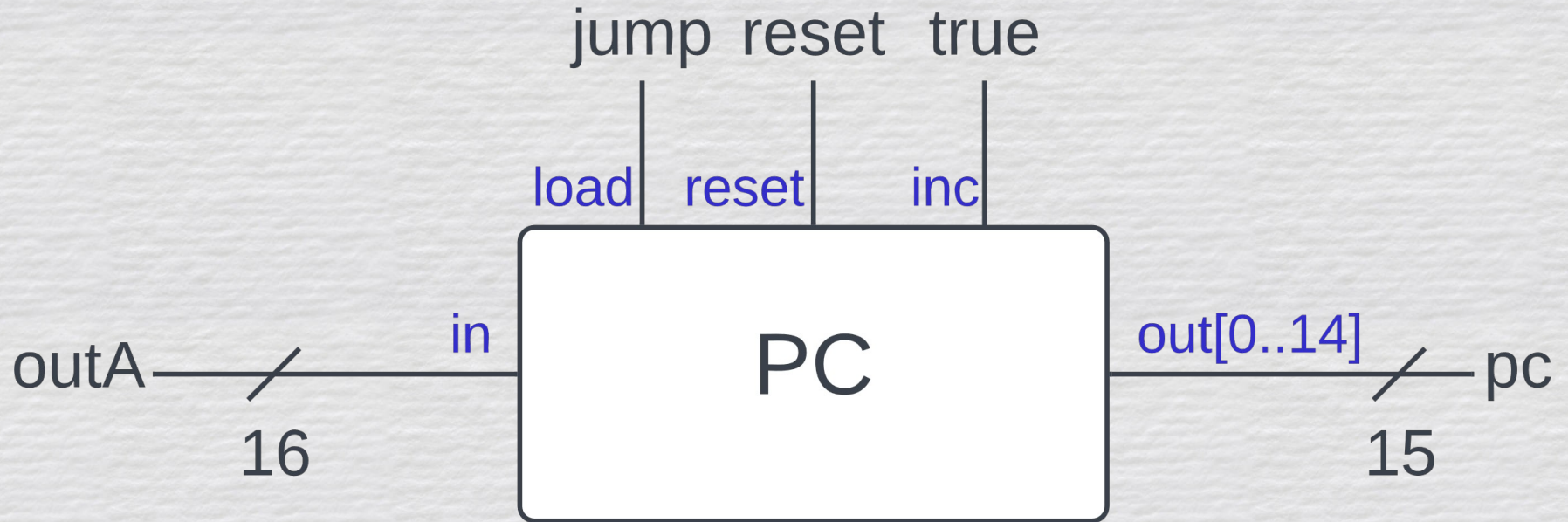


PC Register – Code

```
133 //=====
134 // PC Register
135 /*
136    Takes in the A-Register, jump result, reset input, and increment (always true)
137    to determine where the next address in ROM32K should be
138
139    if (jump == 1)
140    |   pc = outA (we jump to ROM[A])
141    else if (reset == 1)
142    |   pc = 0 (we jump to ROM[0])
143    else
144    |   pc = pc + 1 (we increment to our next address)
145 */
146 PC(in=, load=, reset=, inc=, out[0..14]=);
```


Memory

- The Memory chip is far easier to implement than our CPU
- It simply consists of 3 main components
 - RAM16K
 - Screen
 - Keyboard
- We simply need to use DMuxes and Mux16s to select which of these we would like to use

Memory – Overview

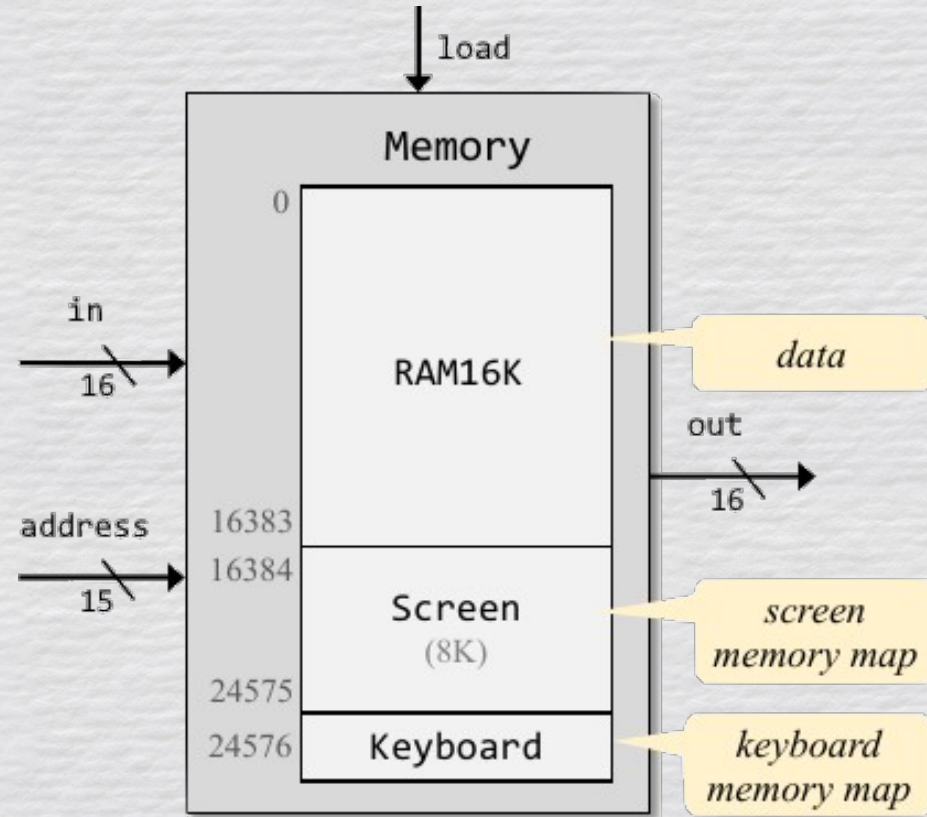


Determine Memory Input

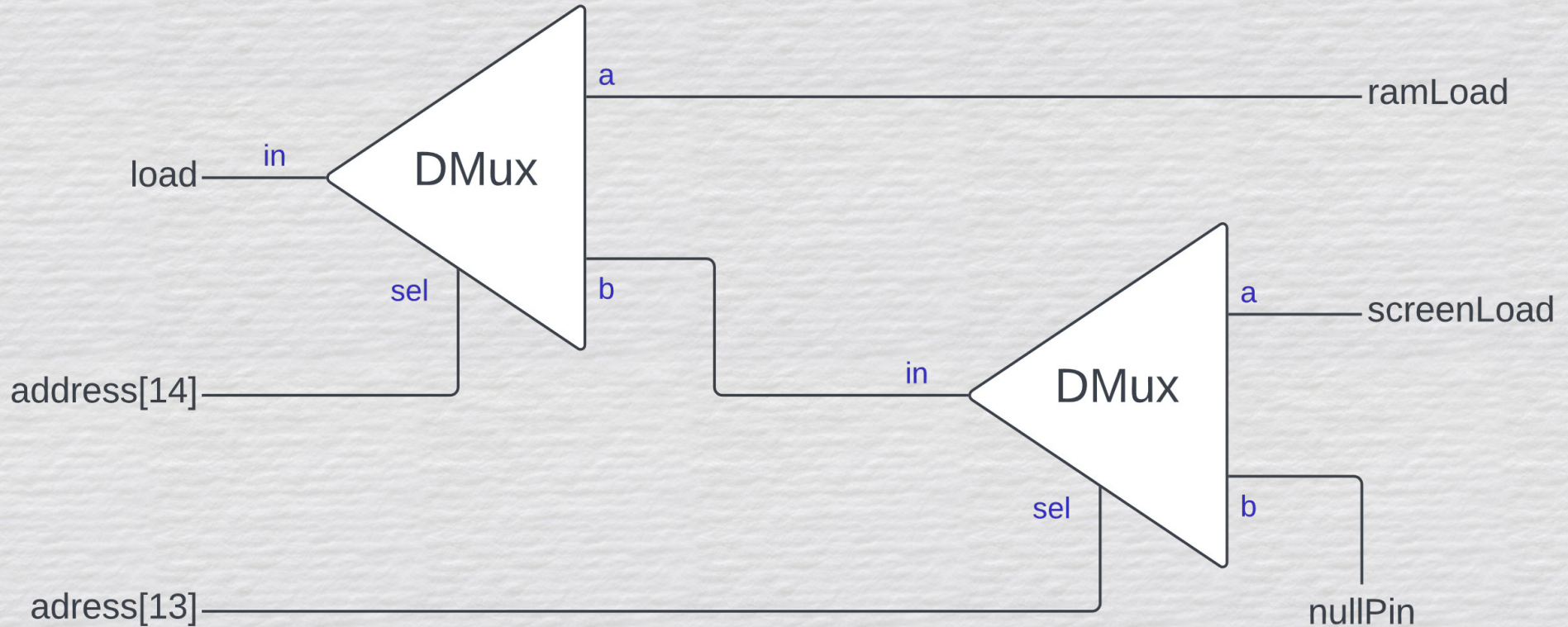


Determine Memory Input – Code

```
30 //=====
31 // Determine Input (DMux)
32 /*
33 |   if (address[14] == 0)
34 |       We are using RAM (ramLoad)
35 |   else
36 |       We are using either Screen or Keyboard (skLoad)
37 */
38 DMux(in= ,sel= ,a= ,b= );
39 /*
40 |   if (address[14] == 1)
41 |   {
42 |       if (address[13] == 0)
43 |           We are using Screen (screenLoad)
44 |       else
45 |           We are using Keyboard and don't use the load input (nullPin)
46 |   }
47 */
48 DMux(in= ,sel= ,a= ,b= );
```


Handle Components – RAM 16K

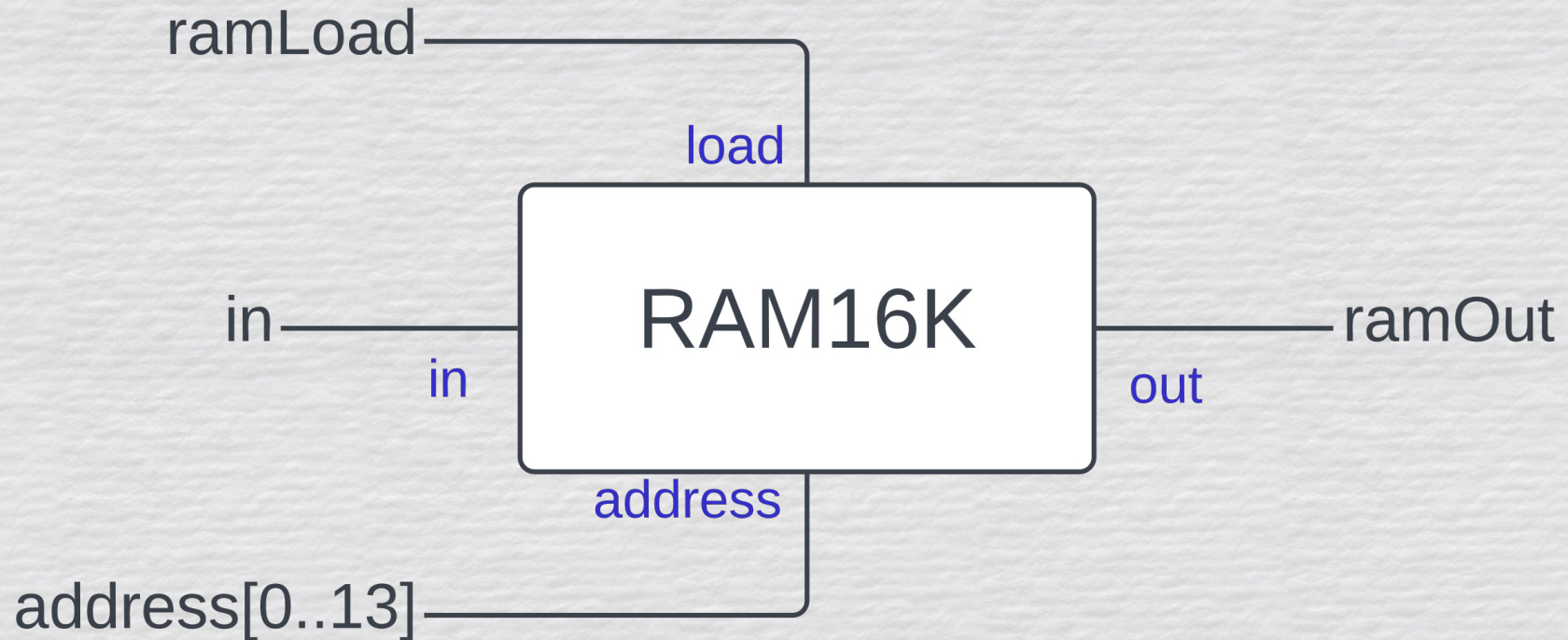

Handle Components – Screen

 


Handle Components – Keyboard

 

Handle Components – Code

```
47 //=====
48 // Handle the outputs of the RAM/Screen/Keyboard
49 // RAM16K using the aforementioned ramLoad and the first 14 bits of the address (ramOut)
50 RAM16K(in=, load=, address=, out=);
51 // Screen (RAM8K) using the aforementioned screen and the first 13 bits of the address (screenOut)
52 Screen(in=, load=, address=, out=);
53 // Simple Keyboard (kbdOut)
54 Keyboard(out=);
```

Determine Memory Output

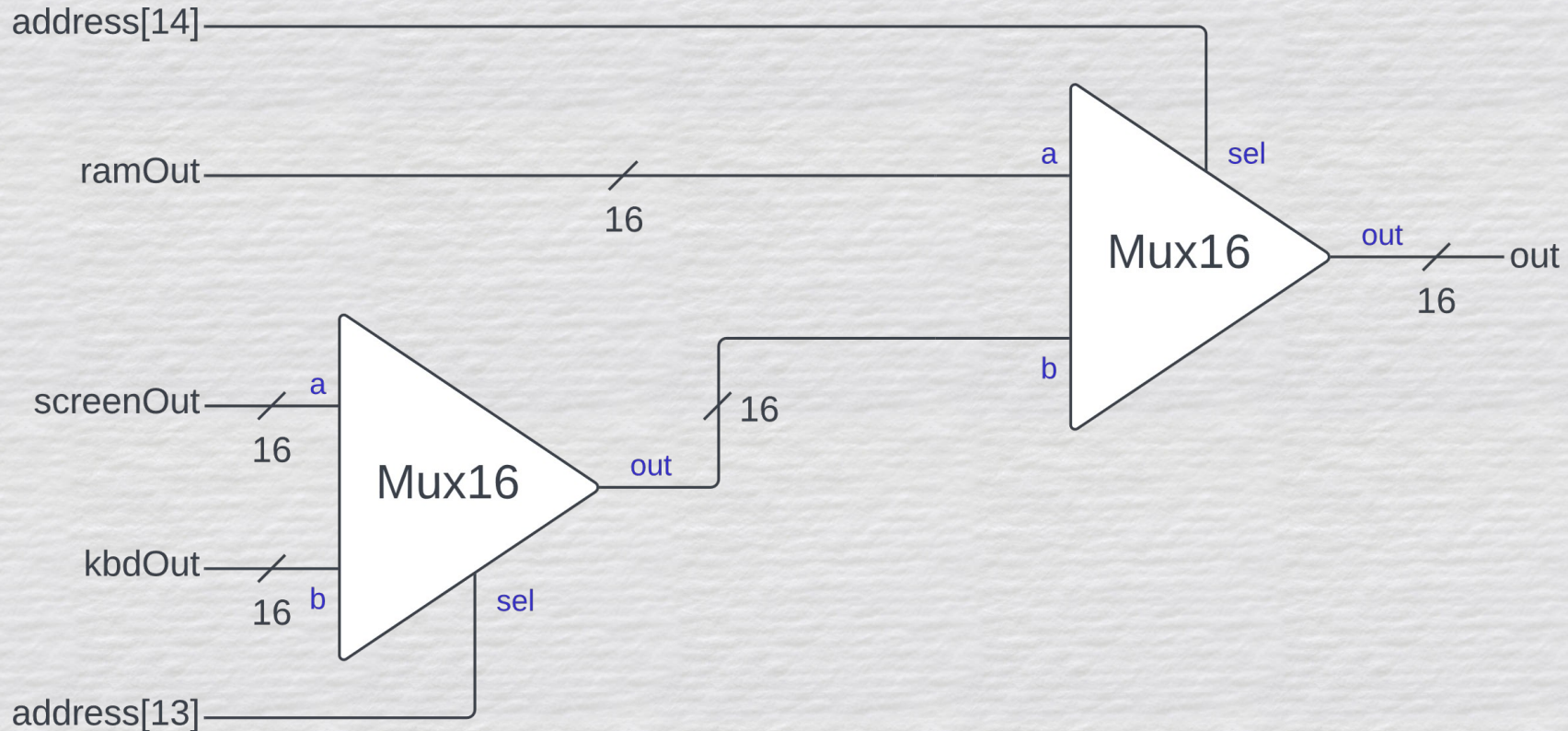

Determine Memory Output – Code

```
59 //=====
60 // Determine Output (Mux16)
61 /*
62     if (address[13] == 0)
63     |   We are using Screen (screenOut)
64     else
65     |   We are using Keyboard (kbdOut)
66 */
67 Mux16(a= ,b= ,sel= ,out= );
68 /*
69     if (address[14] == 0)
70     |   We are using RAM (ramOut)
71     else
72     |   We are using either Screen or Keyboard (skLoad)
73 */
74 Mux16(a= ,b= ,sel= ,out= );
```