

Computer Organization

Introduction to Boolean Logic

Boolean Values

- All data can be broken down to simple binary values
 - 0 / False
 - 1 / True
- These values are used in what is known as Boolean Functions
 - These functions consist of various Boolean Operators such as And, Or, Not, Xor, Nand, etc.

Truth Tables


- All Binary Functions can have their inputs/outputs be represented by truth tables

<i>x</i>	<i>y</i>	And
1	1	1
1	0	0
0	1	0
0	0	0

Boolean Functions – And

- And
 - A function that expects all inputs to be true (functions very similar to basic multiplication)


<i>x</i>	<i>y</i>	And
1	1	1
1	0	0
0	1	0
0	0	0

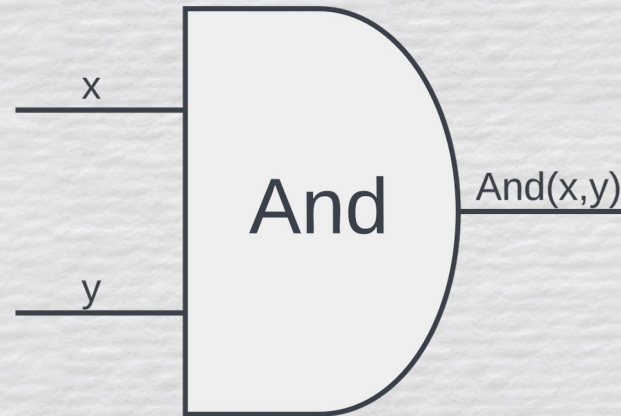

Boolean Functions – Or

- Or
 - A function that expects at least one input to be true (functions very similar to basic addition)


<i>x</i>	<i>y</i>	Or
1	1	1
1	0	1
0	1	1
0	0	0

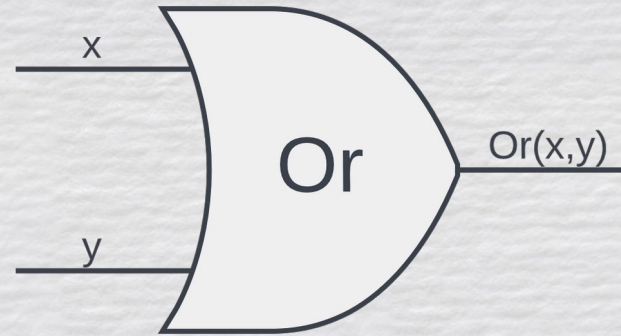

Boolean Functions – Xor

- Xor
 - A function that expects differing inputs


<i>x</i>	<i>y</i>	Xor
1	1	0
1	0	1
0	1	1
0	0	0

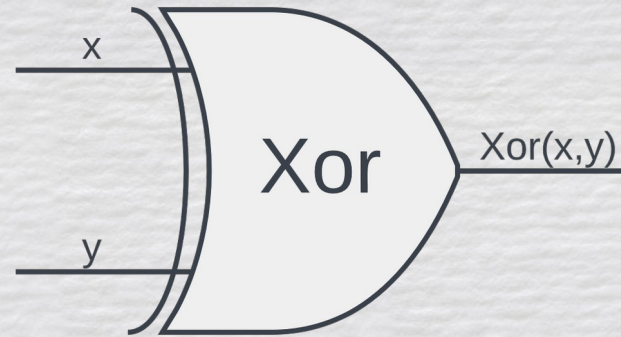

Boolean Functions – Not

- Not
 - A function that outputs the opposite of the input


x	Not
1	0
0	1

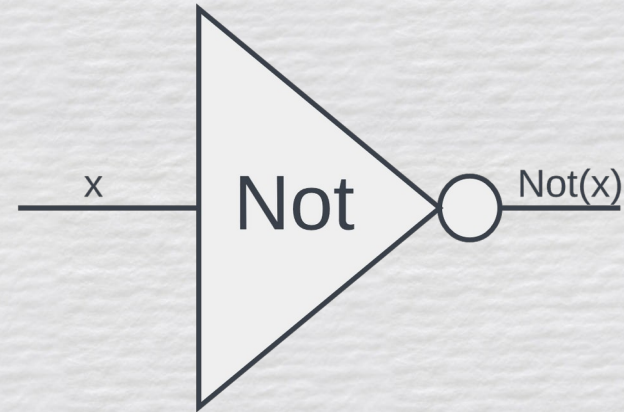

Boolean Functions – Nand

- Nand
 - A negated And function


<i>x</i>	<i>y</i>	Nand
1	1	0
1	0	1
0	1	1
0	0	1

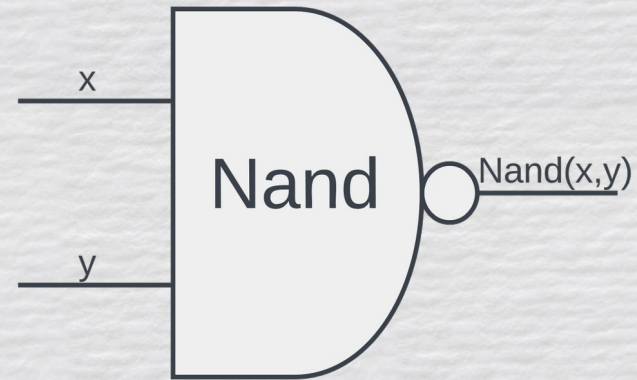

Boolean Functions – Nor

- Nor
 - A negated Or function

<i>x</i>	<i>y</i>	Nor
1	1	0
1	0	0
0	1	0
0	0	1

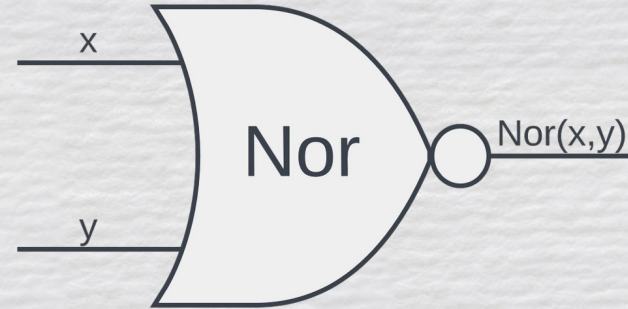

Boolean Functions – Xnor

- Xnor
 - A negated Xor function

x	y	Xnor
1	1	1
1	0	0
0	1	0
0	0	1

