

Computer Organization

Arithmetic Gates

Adding Numbers

- Adding numbers starts from a basic concept
 - Add 2 inputs, get the sum and carry
 - Move to the next to add the next 2 inputs and the previous carry

$$\begin{array}{cccc} & 0 & 0 & 1 & 0 \\ + & 1 & 0 & 1 & 0 \\ \hline & 0 & 0 & 1 & 1 \\ \hline 1 & 1 & 0 & 1 \end{array}$$

Binary addition

$$\begin{array}{cccc} & 0 & 0 & 1 \\ + & 0 & 0 & 0 & 1 \\ \hline & 0 & 1 & 0 & 1 \\ \hline 0 & 1 & 1 & 0 \end{array}$$


Another example

$$\begin{array}{cccc} & 1 & 1 & 1 & 0 \\ + & 0 & 1 & 1 & 1 \\ \hline & 1 & 1 & 1 & 0 \\ \hline 1 & 0 & 1 & 0 & 1 \end{array}$$

Overflow


Half Adder

 - Half Adders take 2 inputs and output a sum and a carry.
 - Used to kick start an addition operation



Full Adder

 - Full Adders are used as the continuous elements of addition operation since they account for carry bits
 - Takes in 2 inputs and a carry input to output a sum and a carry



Add Bit Sequences (Add 16)

- Using half adders and full adders, it's very simple to compute the addition of 2 bit sequences
 - Pass the Least Significant Bit ([0] for the .hdl language) into a Half Adder
 - Pass the rest of the 15 bits and the previous carry bits into Full Adders until you've accounted for all bits

```
6  /**
7   * Adds two 16-bit values.
8   * The most significant carry bit is ignored.
9   */
10
11 CHIP Add16 {
12     IN a[16], b[16];
13     OUT out[16];
14
15     PARTS:
16     // Put your code here:
17     HalfAdder(a=a[0],b=b[0],sum=out[0],carry=carry1);
18     FullAdder(a=a[1],b=b[1],c=carry1,sum=out[1],carry=carry2);
19     ...
20
21     FullAdder(a=a[15],b=b[15],c=carry15,sum=out[15],carry=carry16);
22 }
23
```

 

Incrementing a Bit Sequence (Inc 16)

- Incrementing a bit sequence is incredibly simple
 - Pass the entire first input into an Add-N (16 for our use cases)
 - Then, pass **true** in for the LSB of the next bit sequence and **false** for all other bits
 - This creates **00000000000000001**

```
6  /**
7   * 16-bit incrementer:
8   * out = in + 1 (arithmetic addition)
9   */
10
11 CHIP Inc16 {
12     IN in[16];
13     OUT out[16];
14
15     PARTS:
16     // Put your code here:
17     Add16(a=in,b[0]=true,b[1..15]=false,out=out);
18 }
```


The ALU

- What even is this?




The ALU – cont.

 - The ALU computes a given function on its two given data inputs, and outputs the result
- f : one out of a family of pre-defined arithmetic functions (*add, subtract, multiply, ...*) and logical functions (*And, Or, Xor, ...*)




The Hack ALU

 - Inputs
 - Two 16-bit, two's complement values
 - Six 1-bit control values
- Outputs
 - One 16-bit, two's complement value
 - Two 1-bit values



The Hack ALU – cont.

 - The control bits determine the ALU's function



control bits						
zx	nx	zy	ny	f	no	out
1	0	1	0	1	0	0
1	1	1	1	1	1	1
1	1	1	0	1	0	-1
0	0	1	1	0	0	x
1	1	0	0	0	0	y
0	0	1	1	0	1	!x
1	1	0	0	0	1	!y
0	0	1	1	1	1	-x
1	1	0	0	1	1	-y
0	1	1	1	1	1	x+1
1	1	0	1	1	1	y+1
0	0	1	1	1	0	x-1
1	1	0	0	1	0	y-1
0	0	0	0	1	0	x+y
0	1	0	0	1	1	x-y
0	0	0	1	1	1	y-x
0	0	0	0	0	0	x&y
0	1	0	1	0	1	x y

The Control Bits

- We can treat the 6 control bits as if statements that string together to form a single function
- But how do we do this in hardware?


pre-setting the x input		pre-setting the y input		selecting between computing + or &	post-setting the output	Resulting ALU output
zx	nx	zy	ny	f	no	out
if zx then x=0	if nx then x=!x	if zy then y=0	if ny then y=!y	if f then out=x+y else out=x&y	if no then out=!out	out(x,y)=
1	0	1	0	1	0	0
1	1	1	1	1	1	1
1	1	1	0	1	0	-1
0	0	1	1	0	0	x
1	1	0	0	0	0	y
0	0	1	1	0	1	!x
1	1	0	0	0	1	!y
0	0	1	1	1	1	-x
1	1	0	0	1	1	-y
0	1	1	1	1	1	x+1
1	1	0	1	1	1	y+1
0	0	1	1	1	0	x-1
1	1	0	0	1	0	y-1
0	0	0	0	1	0	x+y
0	1	0	0	1	1	x-y
0	0	0	1	1	1	y-x
0	0	0	0	0	0	x&y
0	1	0	1	0	1	x y

The Control Bits – cont.


- We can treat the 6 control bits as if statements that string together to form a single function
- But how do we do this in hardware? **Muxes**

pre-setting the x input		pre-setting the y input		selecting between computing + or &	post-setting the output	Resulting ALU output
zx	nx	zy	ny	f	no	out
if zx then x=0	if nx then x=!x	if zy then y=0	if ny then y=!y	if f then out=x+y else out=x&y	if no then out=!out	out(x,y)=
1	0	1	0	1	0	0
1	1	1	1	1	1	1
1	1	1	0	1	0	-1
0	0	1	1	0	0	x
1	1	0	0	0	0	y
0	0	1	1	0	1	!x
1	1	0	0	0	1	!y
0	0	1	1	1	1	-x
1	1	0	0	1	1	-y
0	1	1	1	1	1	x+1
1	1	0	1	1	1	y+1
0	0	1	1	1	0	x-1
1	1	0	0	1	0	y-1
0	0	0	0	1	0	x+y
0	1	0	0	1	1	x-y
0	0	0	1	1	1	y-x
0	0	0	0	0	0	x&y
0	1	0	1	0	1	x y


The Control Bits: A Thrilling Series – 1

 


The Control Bits: A Thrilling Series – 2

 


The Control Bits: A Thrilling Series – 3

 

The Control Bits: A Thrilling Series – 4

 

The ALU: NoStat

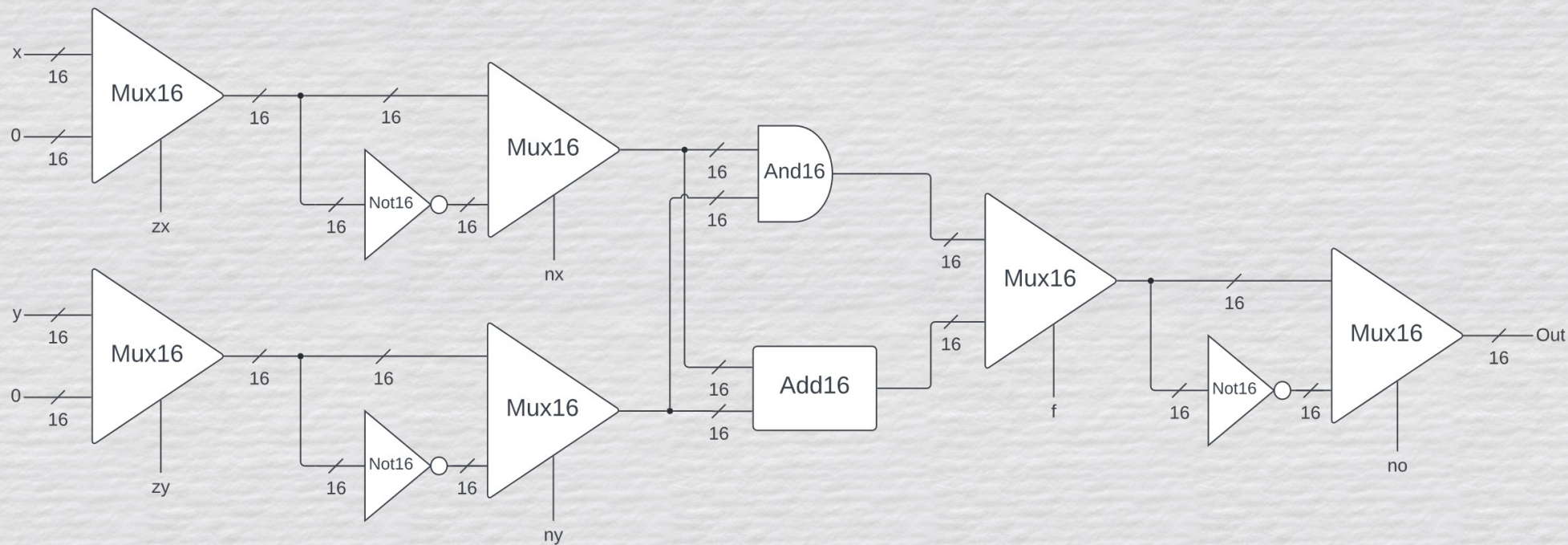

The ALU

