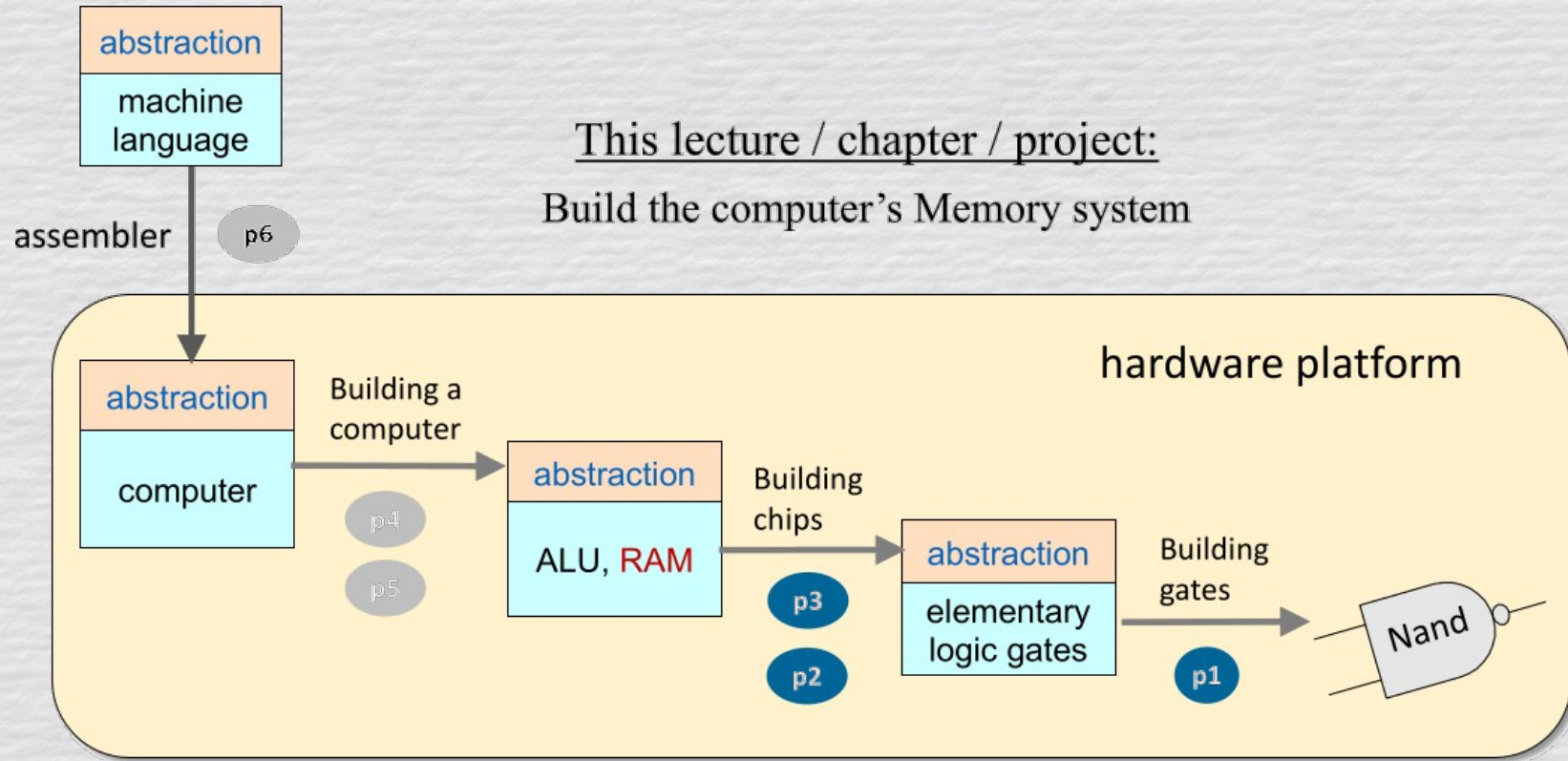


Computer Organization

Sequential Logic

Roadmap



Simple Model - Complex System

- A very common theme that occurs in computer science
- We first design a simple model
 - Logic Gates for this course
- We then proceed to add various layers of abstraction to build up to a more complex system

Combinational Logic

- During the course of Chapter 1, we developed several logic gates including some fairly complex multiplexors
- During Chapter 2, we extended this even further by designing a fairly robust ALU
 - A very simple ALU, but quite elegant in design thanks to the abstractions of Two's Complement and Boolean Logic

Combinational Logic – cont.

- While the current setup we have is quite clever, it is still fairly limited
- We can compute various operations on a fixed number of inputs
 - And16, Dmux8Way, Add16, ALU, etc.
- We cannot do this for a dynamic number of inputs though...

Sequential Logic


- The answer to our issue is time
- Our current gates are completely time-independent in their current state, but we can solve that via sequential logic
- This allows us to pass the output of our gates back to their inputs giving us a way to track changes over time

Sequential Logic – Software

- Software
 - The ability to store data
 - $x = 17$
 - `int i = 0`
 - The ability to solve things sequentially
 - Loops
 - Recursion


Sequential Logic – Hardware

 - Hardware
 - Must be able to handle physical hardware delays when moving data from one chip to another




Discrete Time

 - Set time cycle slightly greater than maximum delay
- Use outputs only at end of cycle
 - Ignore changes between




Discrete Time – Ideal

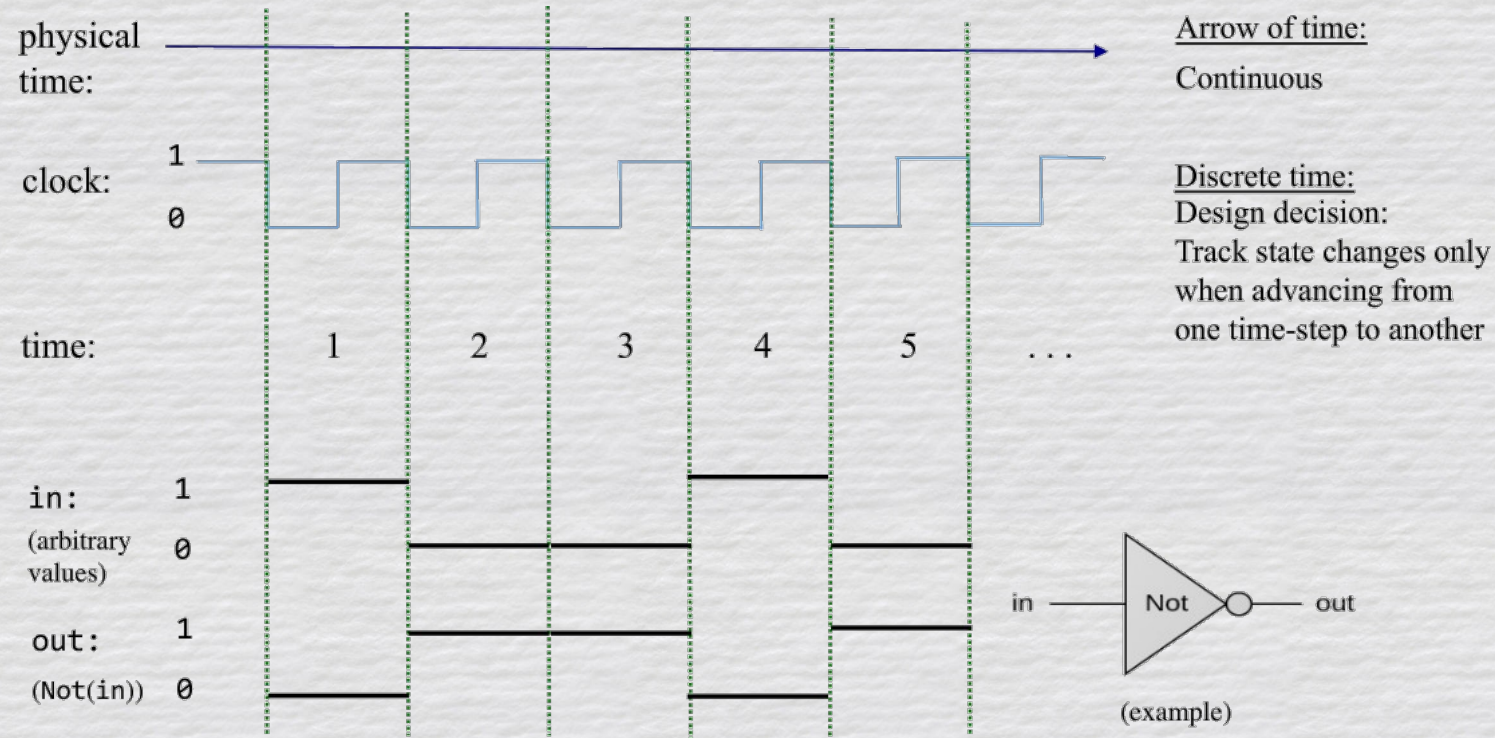


Desired / idealized behavior of the in and out signals:

That's how we *want* the hardware to behave

Discrete Time – Actual

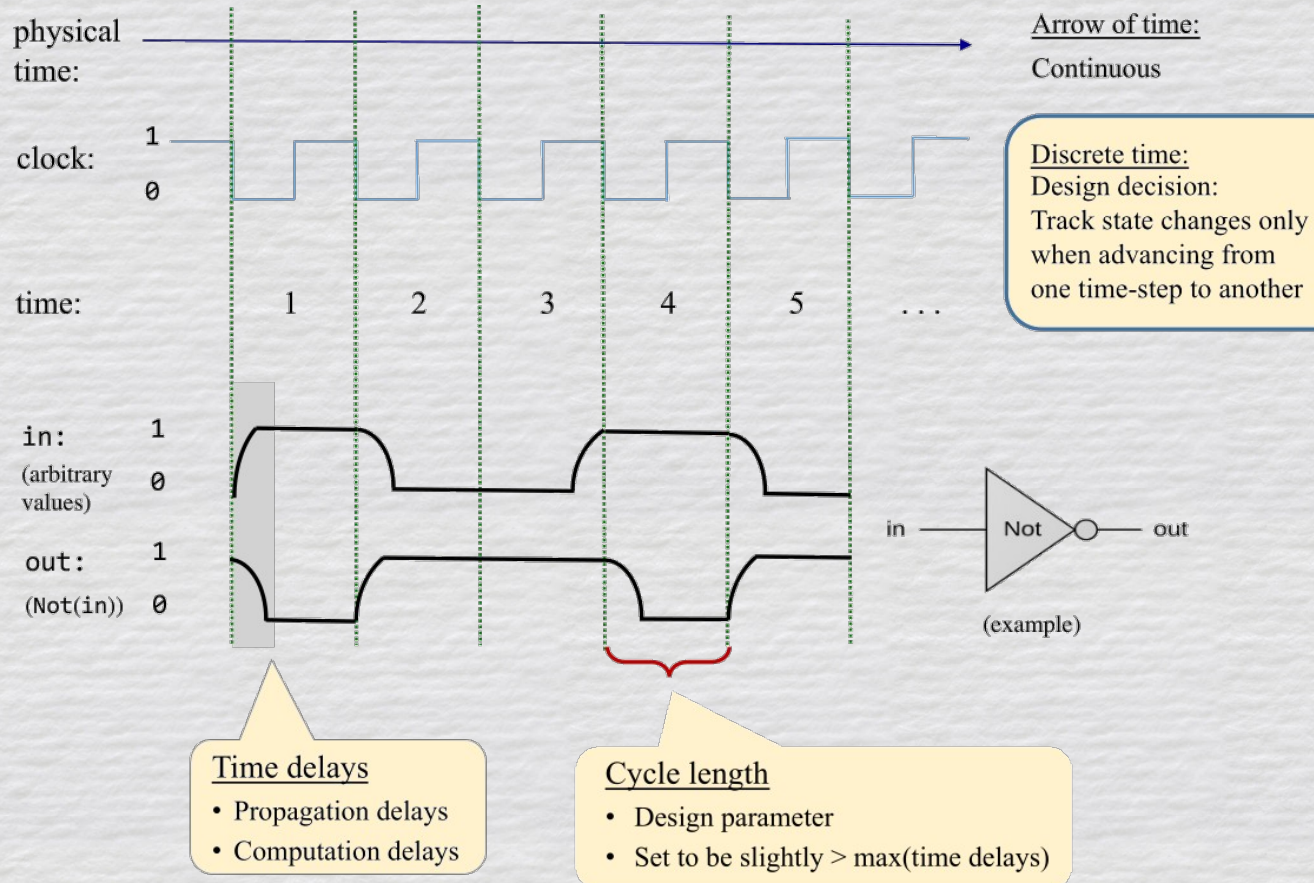


Discrete Time – Results

 

Resulting effect:

- Combinational chips react “immediately” to their inputs
- Facilitated by the decision to track changes only at cycle ends

Memory Hierarchy

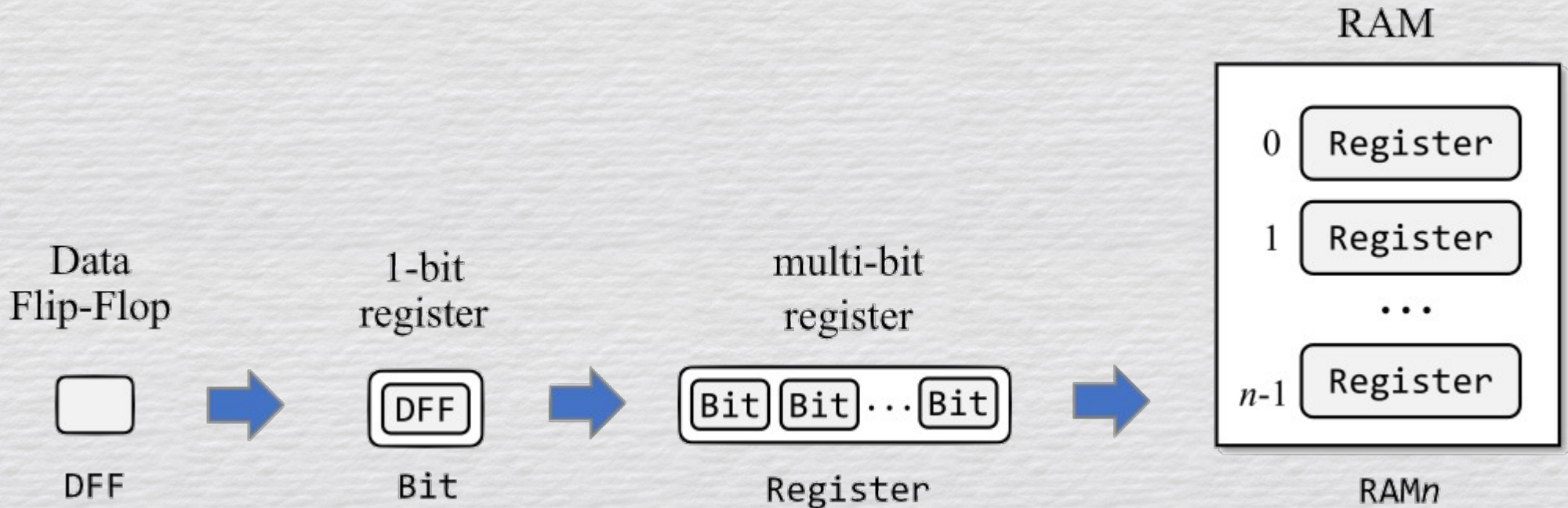


Data Flip Flop

Data Flip Flop (aka *latch*)


The most elementary sequential gate: Outputs the input in the previous time-step



$$\text{out}(t) = \text{in}(t-1)$$

 

Register

 

Basic abstractions:

- “Loading” a value
- “Storing” a value

1 2 3 4 5 6 7 ... 205 206 207 208 209 210 211 ...

x = 17 , 17, 17, 17, 17, 17, 17, ... ,

loading

storing

x = 21 , 21, 21, 21, 21, 21, 21, ...

loading

storing

time

(cycles)